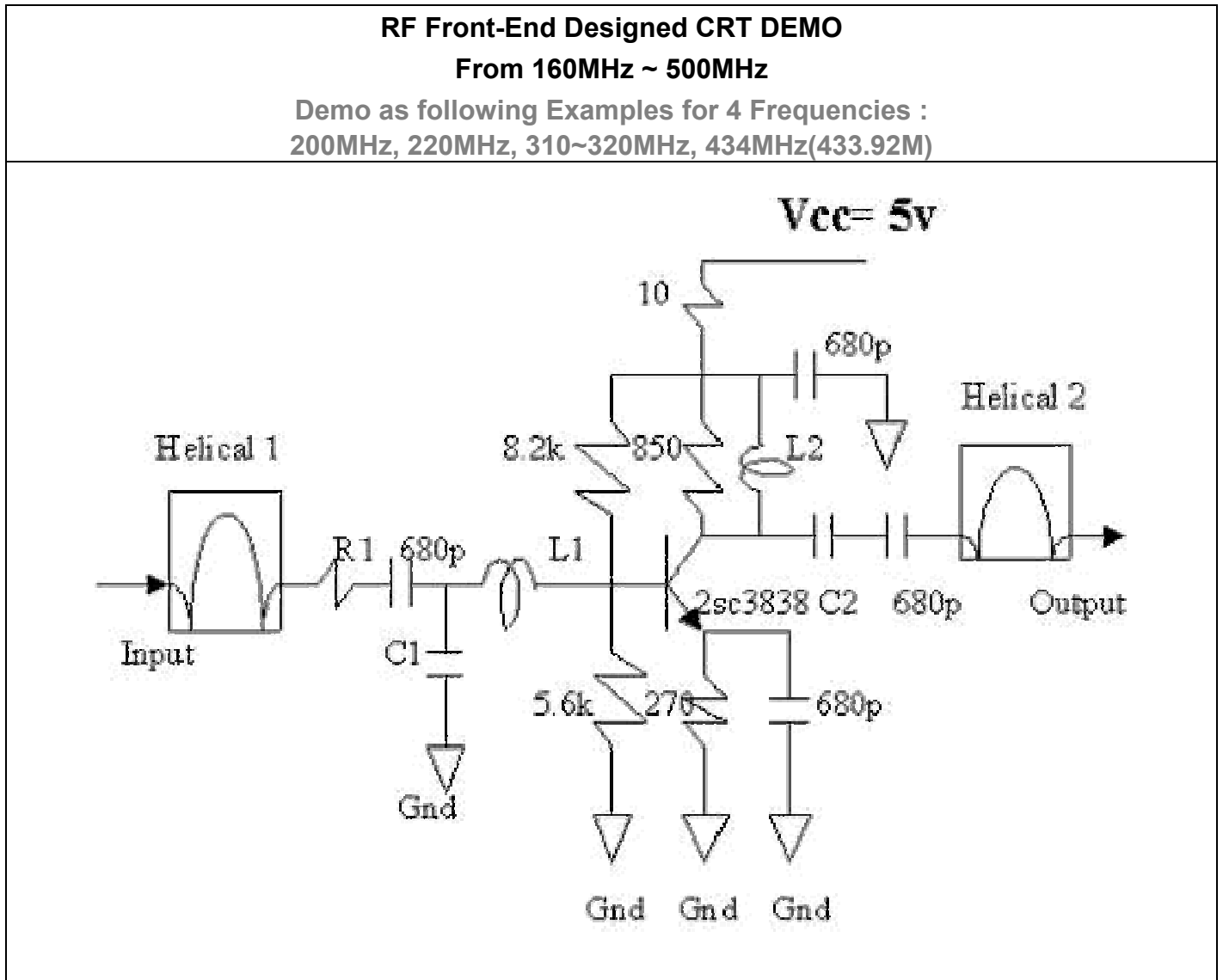


RF Front-End Designed CRT DEMO

(1)Application Circuit



(2) Parts List :

Rx Freq.	Helical 1	R1	C1	L1	C2	L2	Helical 2
200 MHz	TD6732B-200M	10Ω	27pf	40nH	4pf	66nH	TD6732B-200M
220MHz	TD6732B-220M	10Ω	27pf	40nH	4pf	66nH	TD6732B-220M
318MHz	TD6710B-318M		17pf	25nH	5pf	27nH	TD6710B-318M
434MHz	TD6711B-434M		10pf	14nH	5pf	18nH	TD6711B-434M